

CSE 260M - Quiz 8

November 1, 2006

Name: _____

Student ID Number: _____

1. Implement the Finite-State Machine (FSM) defined by the state diagram shown below. The machine has one input "I" and one output "O." Do not worry at this point about resetting the machine. The notation is of the form "Input/Output." Draw your circuit, and be neat.

